
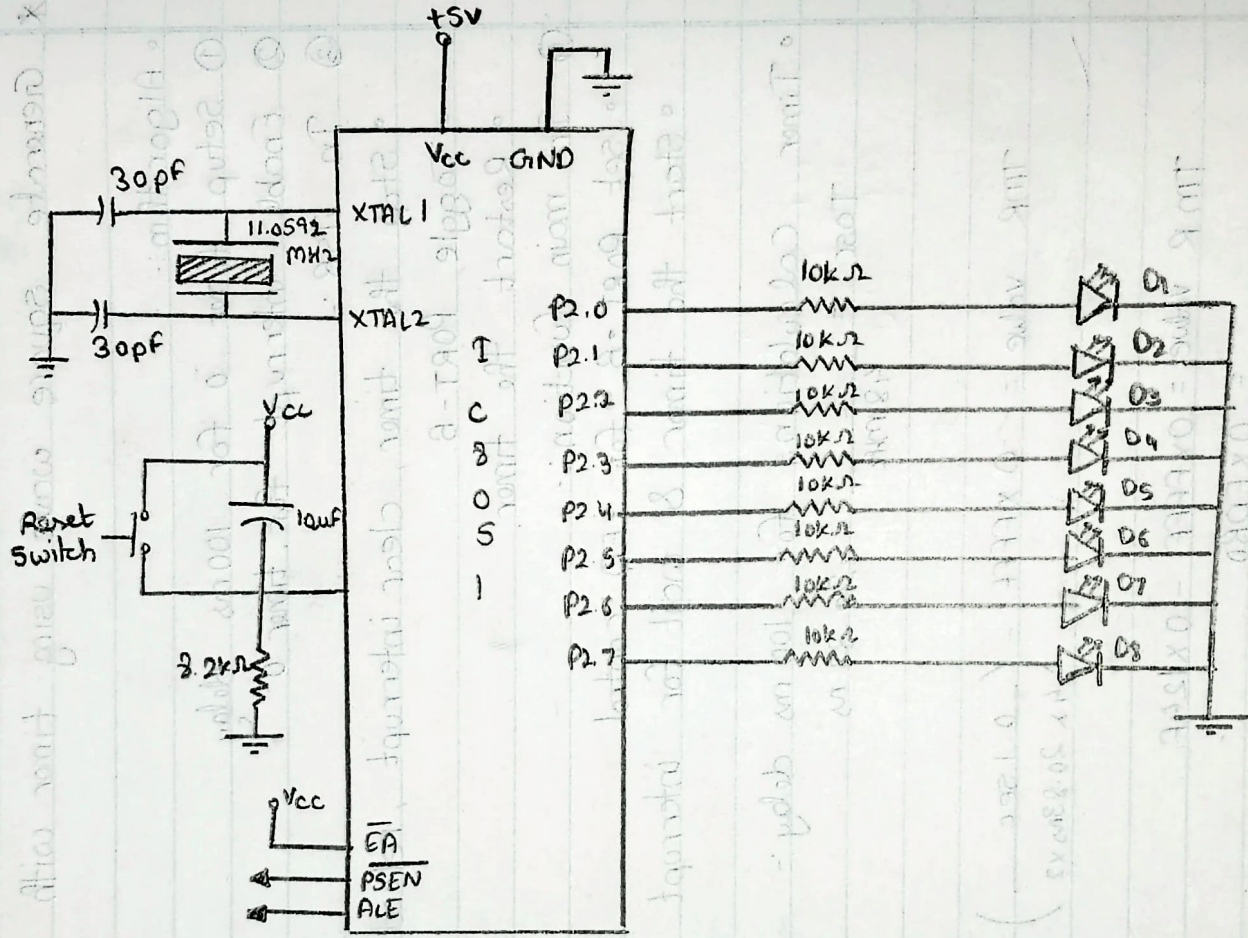


# Interfacing LED with 8051:-

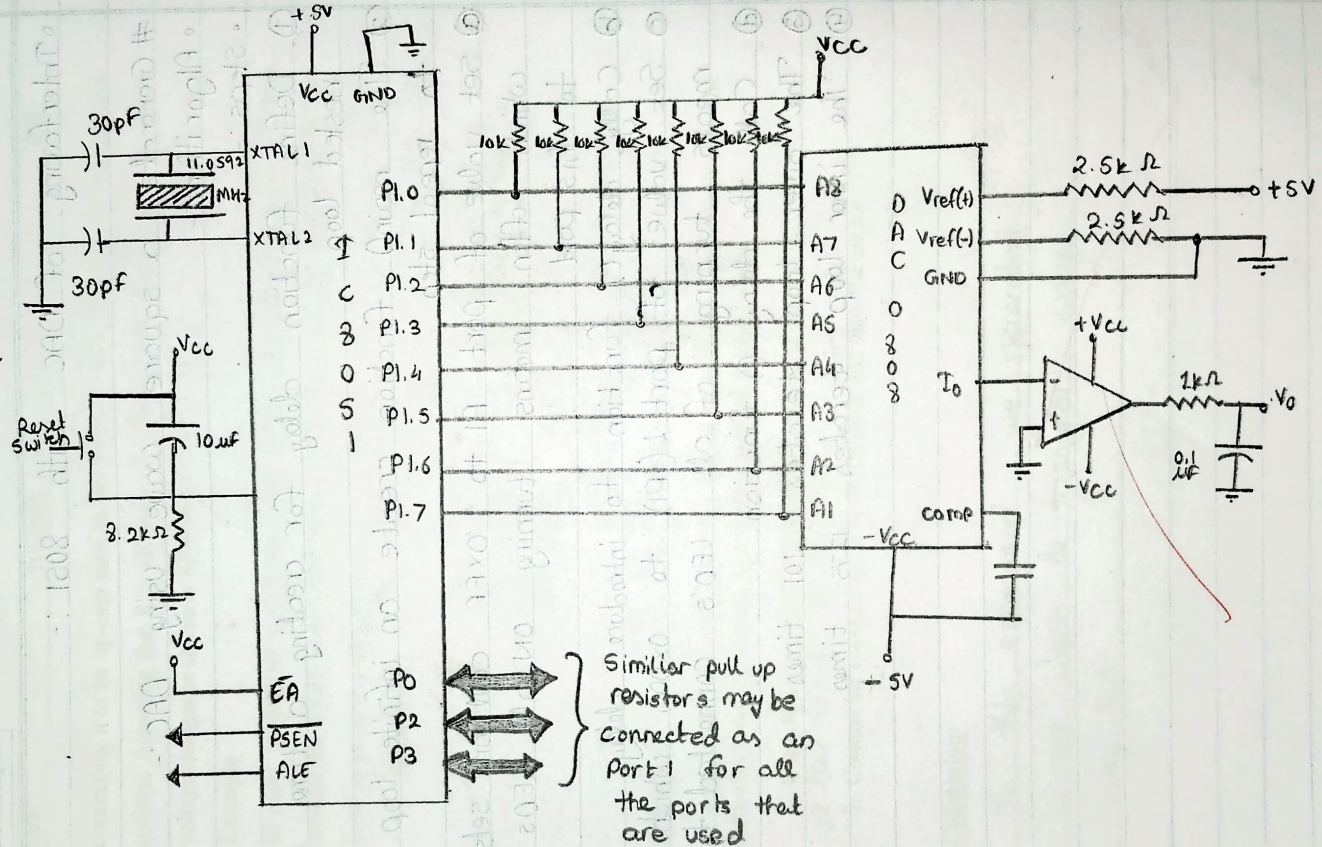


# Interfacing of DAC 0808 with 8051 :-





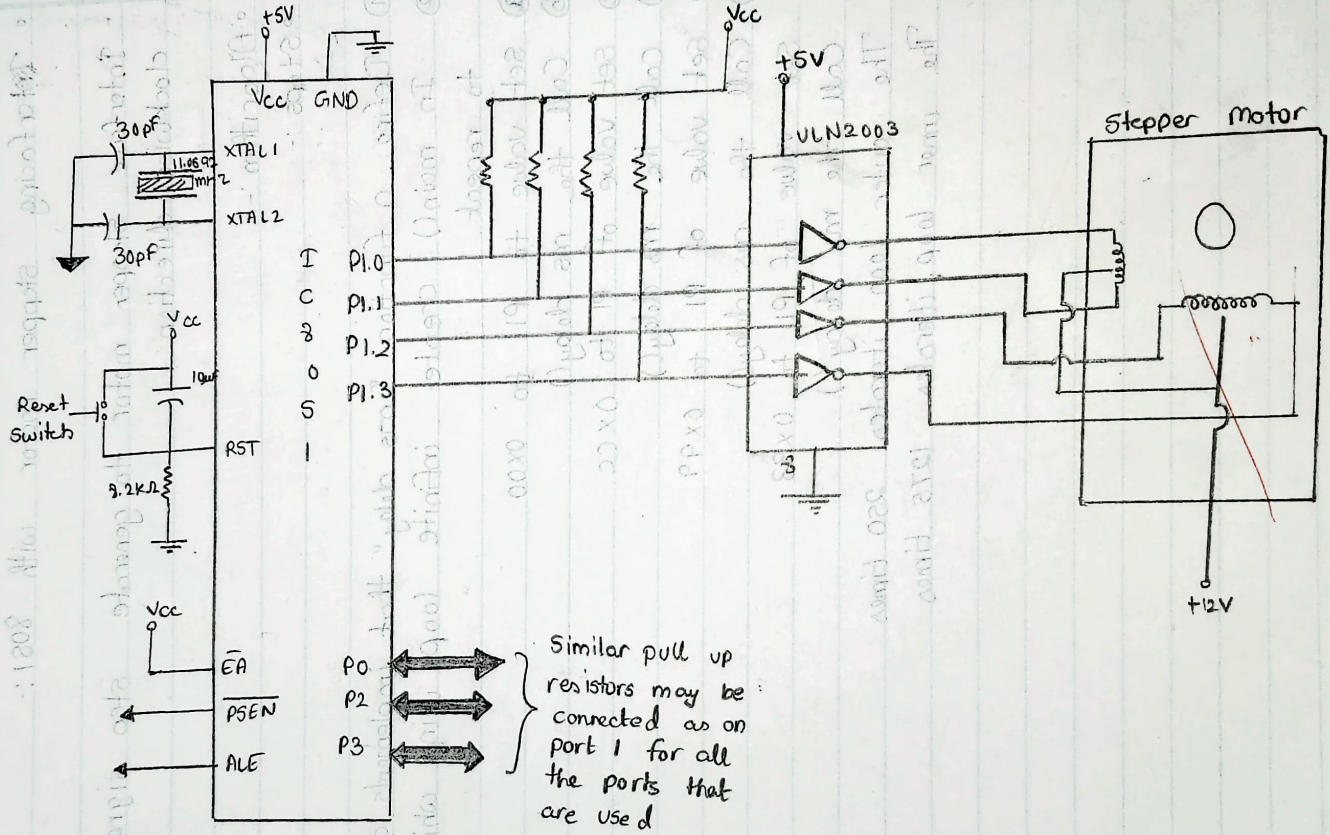
# • Interfacing of Stepper motor with 8051 :-




Similar pull up resistors may be connected as on port 1 for all the ports that are used

# Interfacing LED with PIC18F4550

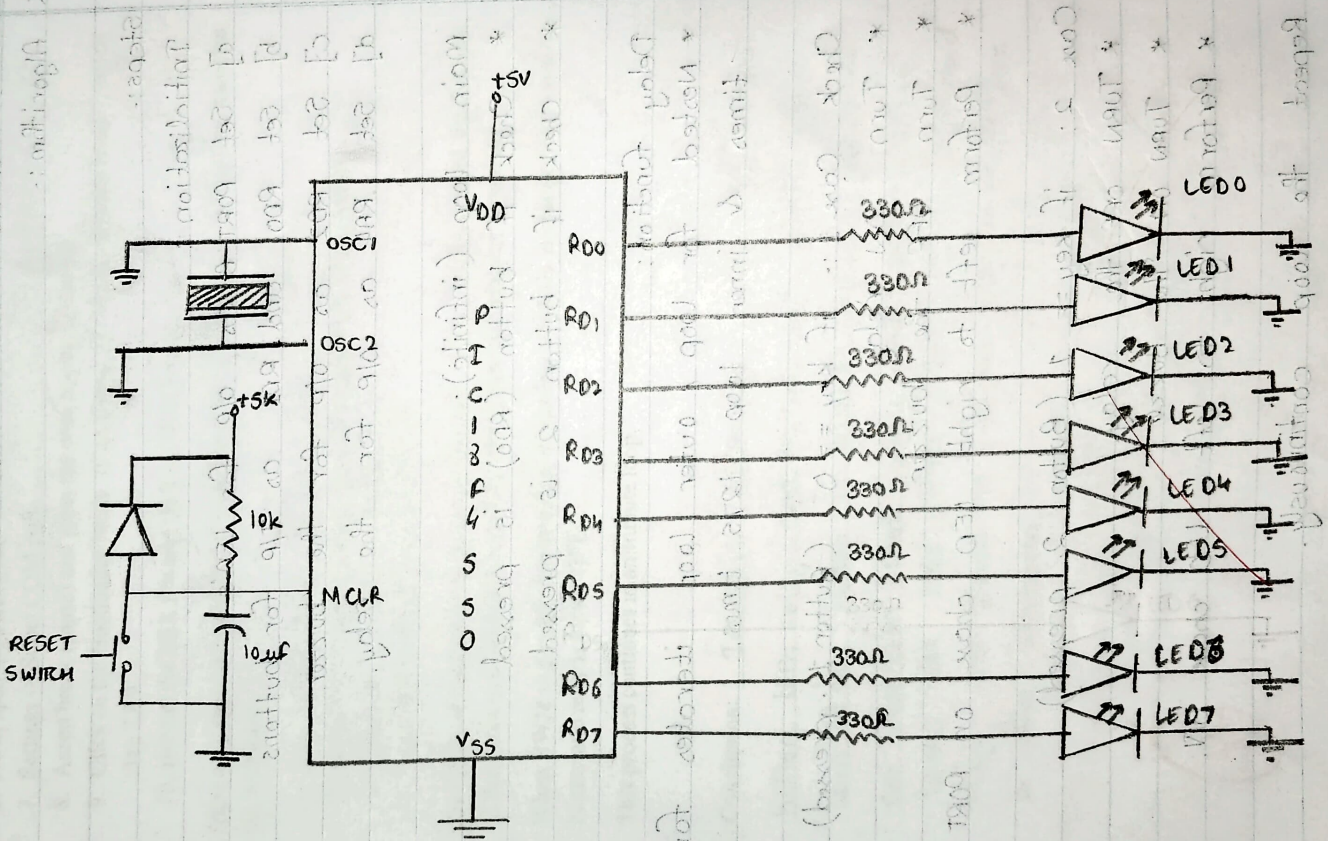




Interfacing 16x2 LCD with PIC18F4550

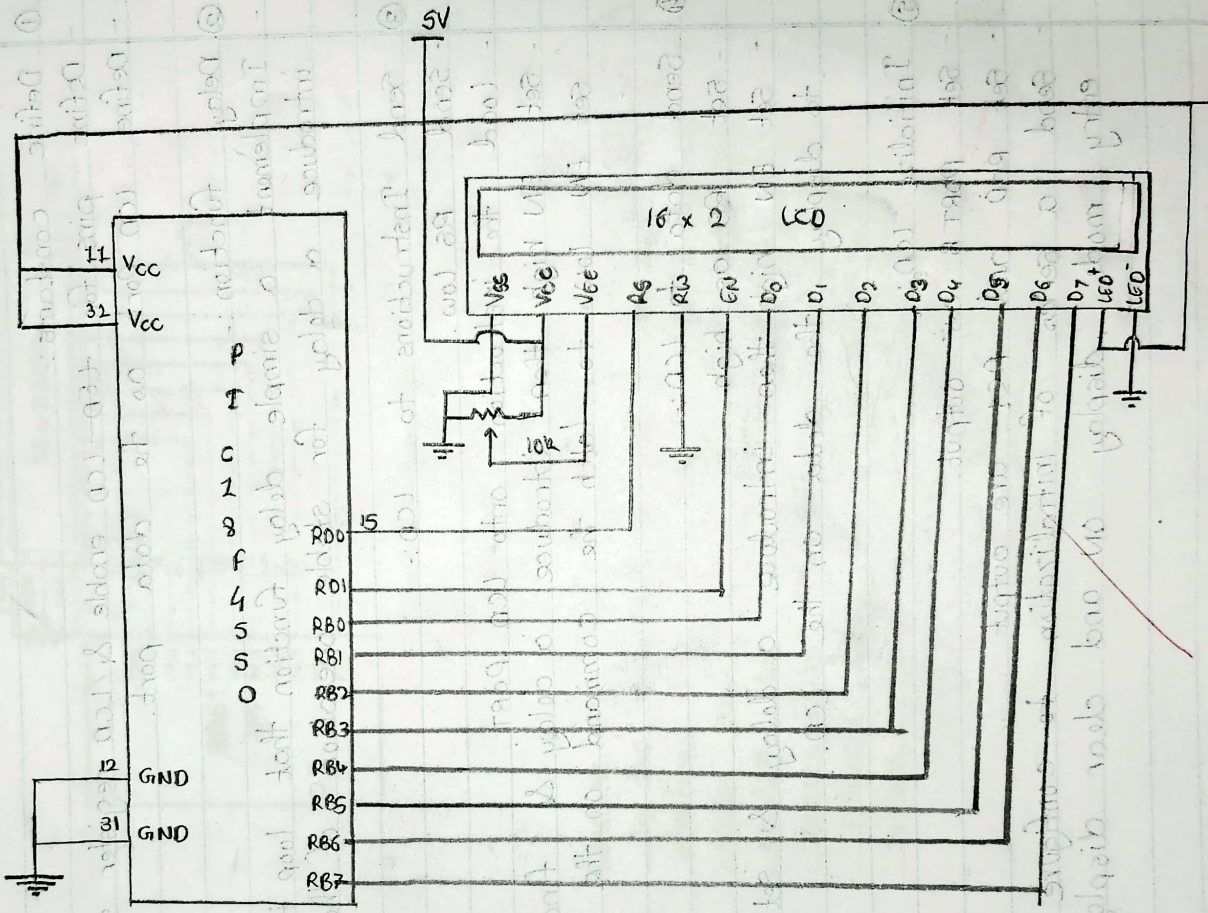


# Interfacing Diagram :-

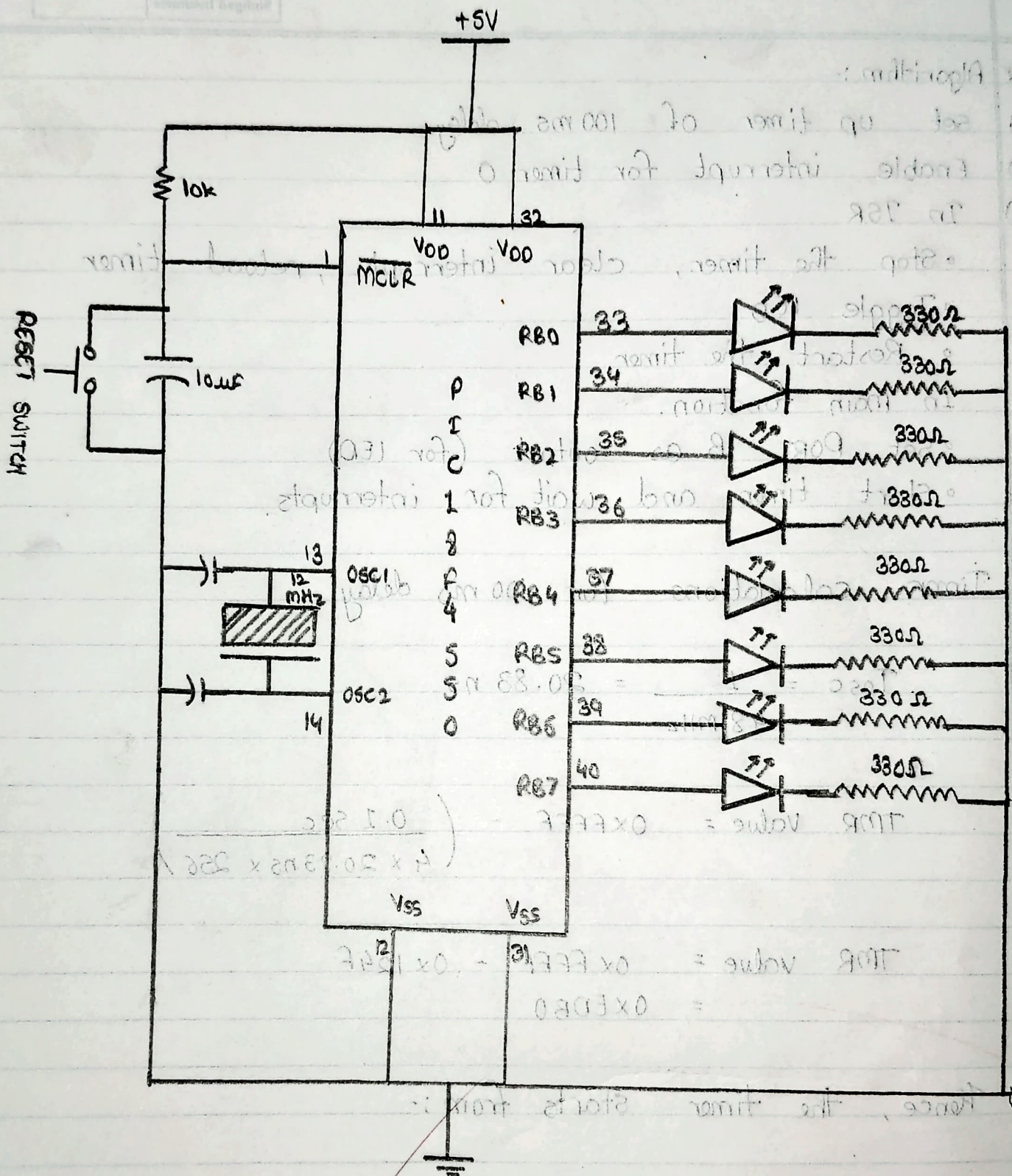



# ◦ Interfacing Diagram :-

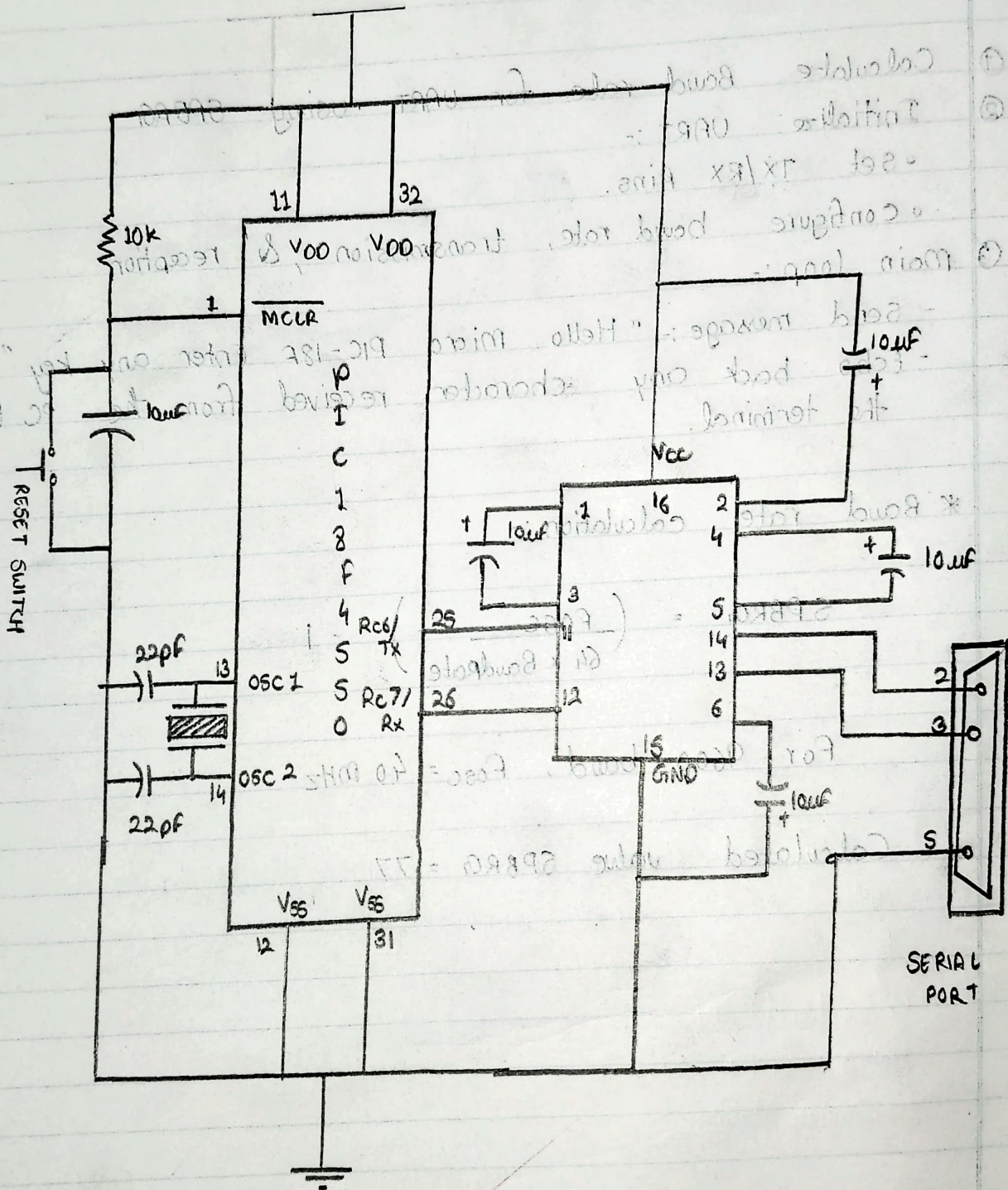



CH53 : CH50

